


BRAC UNIVERSITY
Department of Computer Science & Engineering
Practice Problem sheet (Week 2)
CSE 350: Digital Electronics and Pulse Technique

-
- Use activation voltage V_γ (diode) = 0.6V, V_γ (transistor) = 0.5V, V_{BE} (forward active) = 0.7V, $V_D = 0.7V$ and V_{BE} (sat) = 0.8 V for all the questions.
-

Question No. 1

For the given RTL inverter circuit assume $V_{OH}=10$ V and $V_{OL}=0.2$ V. Also assume common emitter current gain, $\beta_F=30$. Assume for saturation mode $V_{BE}=0.8$ V, $V_{CE}=0.2$ V and cut in voltage for transistor $V_\gamma=0.5$ V.

(a)	Find the Maximum possible Fanout.
(b)	Find the value of V_o if Fanout, $N=2$ (2 Load gates are connected) and input of Driver is Low.
(c)	If V_{in} = High, find the power dissipation in the Driver circuit. (assume No Loads are connected)
(d)	If V_{in} = High, find the power dissipation in the Driver circuit. (assume 50 Loads are connected)
(e)	If V_{in} = Low and Fanout is 2, find the power dissipation in the Driver circuit.

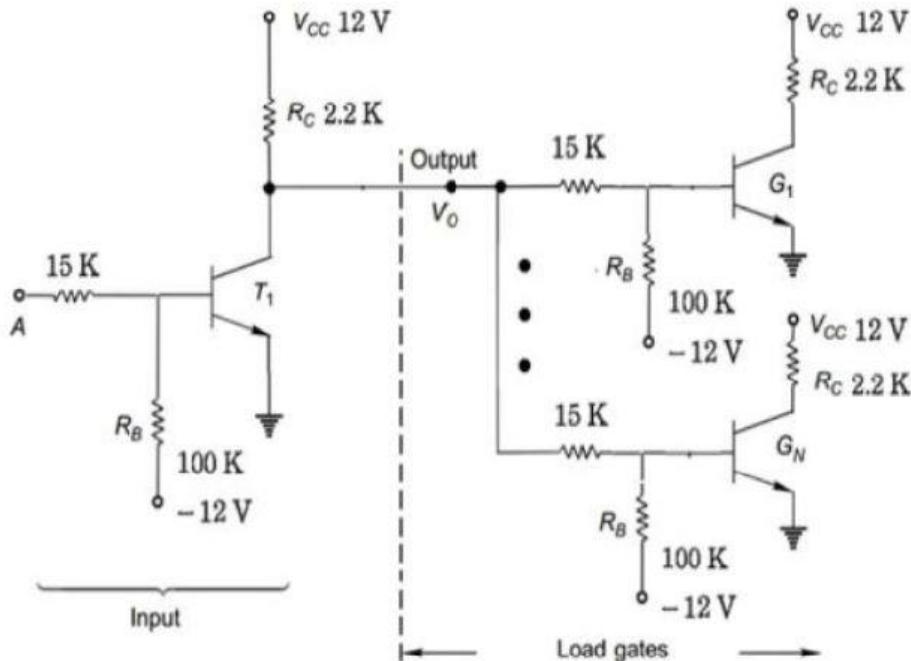

Solution:

(a) Case 1:

$$V_{in} = \text{High} = 12V$$

T_1 sat

$$\therefore V_{c1} = 0.2 = V_0$$

\therefore Input of Load Gates (h_1, \dots, h_N)

$$= V_0 = 0.2 = \text{Low}$$

$\therefore h_1, \dots, h_N$ in cutoff.

$$\text{Now, } I_{RC} = \frac{12 - V_0}{R_C} = \frac{12 - 0.2}{2.2K} = 5.3636 \text{ mA}$$

We will Assume $I_C = 0 \rightarrow$ To maximize I_S .


$$\therefore I_{\text{Supply}} = I_S = I_{RC} = 5.3636 \text{ mA}$$

$$\therefore \text{Individual Load current} = I_L = I_{L1} = \frac{V_0 - (-12)}{(100+15)k\Omega} = \frac{12.2}{115k\Omega} = 0.106 \text{ mA}$$

$$\therefore \text{Total Demand} \quad \text{=} N I_L = N (0.106) \text{ mA}$$

$$I_{\text{Supply}} = I_{\text{Demand}} \rightarrow 5.3636 \text{ mA} = N (0.106 \text{ mA}) \rightarrow N = 50.6$$

└ Floor $\rightarrow N = 50$.

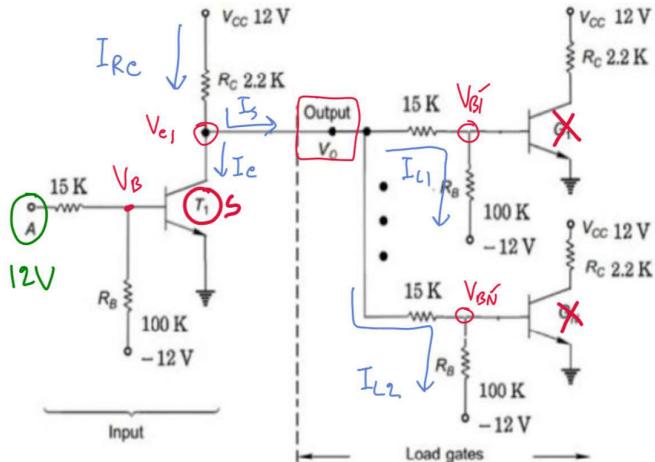

Case 02:


$$V_{in} = \text{Low} = 0.2$$

T_1 in cutoff.

$\therefore V_o = \text{High}$

$\therefore V_{in}$ of Load Gates is High

$\therefore G_1 \dots G_N$ in saturation

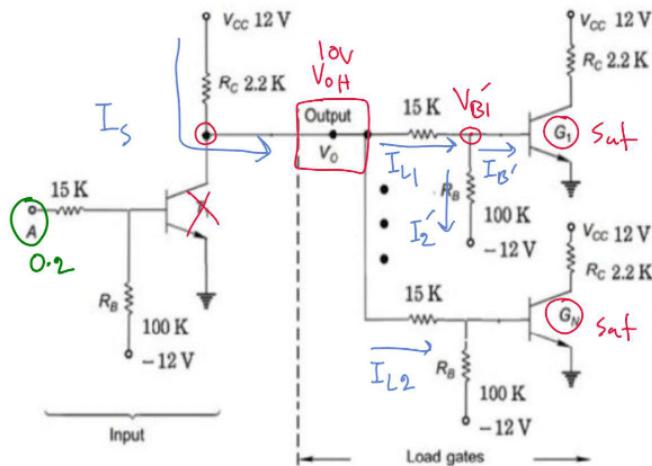

$$\text{Now, } V_o = \text{High} = V_{oH} = 10V$$

$$\text{As } G_1 \text{ in sat} \rightarrow V_{B1'} = 0.8V$$

$$\therefore \text{Individual load current, } I_{L1} = \frac{V_o - V_{B1'}}{15k\Omega} = \frac{10 - 0.8}{15k\Omega} = 0.6133mA$$

$$\text{Supply current} \rightarrow I_s = \frac{12 - 10}{2.2k\Omega} = 0.909mA$$

$$\therefore \text{Supply} = \text{Demand} \rightarrow I_s = N(I_L) \rightarrow 0.909 = N(0.6133)$$

$$\rightarrow N = 1.48$$

$$\hookrightarrow \text{Floor} \rightarrow N = 1.$$

$$\therefore \text{Fanout} = \text{Min}(G_1, 2) = 1 \quad \boxed{\text{Ans}}$$

(b) Find the value of V_o if Fanout, $N=2$ (2 Load gates are connected) and input of Driver is Low.

(b) Given, Fanout = $N = 2$

$$V_{in} = \text{Low} = 0.2V$$


$\therefore T_1$ cutoff

$V_o = \text{High}$

$\therefore G_1 \dots G_N$ in saturation

Now,
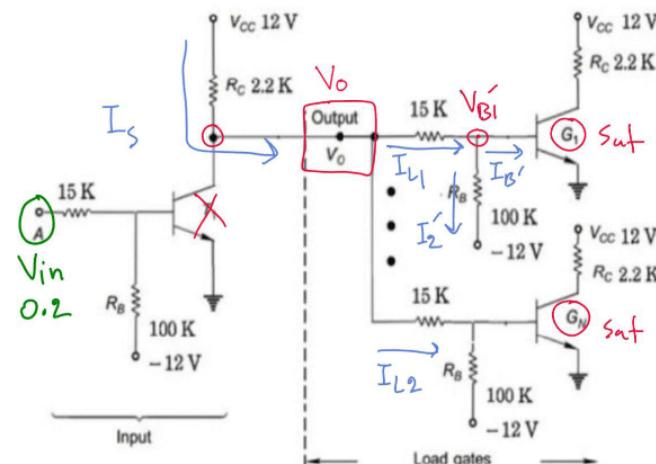
$$\text{Supply} \rightarrow I_s = \frac{12 - V_o}{2.2k\Omega}$$



$$\text{Individual load currents, } I_{L1} = \frac{V_o - V_{B1'}}{15k\Omega} \quad V_o - 0.8$$

(c) If $V_{in} = \text{High}$, find the power dissipation in the Driver circuit. (assume No Loads are connected)

Ans: $V_{in} = 12$

$\therefore T_1$ in sat.

$\therefore V_B = 0.8, V_C = 0.2$

$$\text{Now, } I_1 = \frac{12 - 0.8}{15\text{k}\Omega} = 0.747\text{mA}$$

$$I_2 = \frac{0.8 - (-12)}{100\text{k}\Omega} = 0.128\text{mA}$$



$$I_B = I_1 - I_2 = 0.619\text{mA}$$

$I_S = 0 \rightarrow \{ \text{No Loads are connected} \}$

$$I_{RC} = I_C = \frac{12 - 0.2}{2.2\text{k}\Omega} = 5.3636\text{mA}$$

$\therefore \text{Power} = \sum I \Delta V$
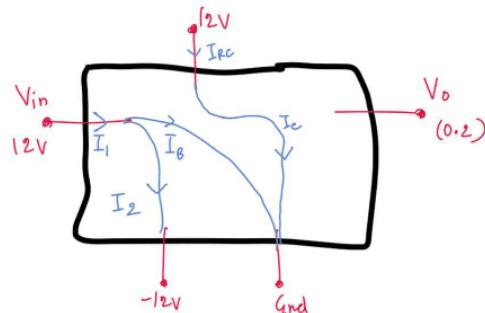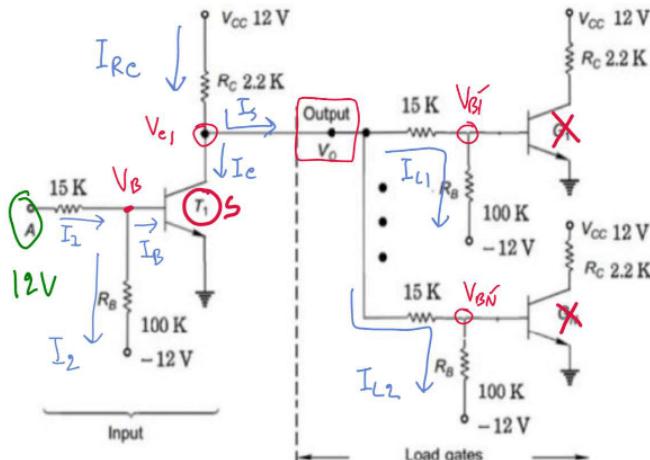
$$\begin{aligned} &= I_2(12 + 12) \\ &+ I_B(12 - 0) + I_C(12 - 0) \\ &= 74.8632\text{mW.} \end{aligned}$$



(d) If $V_{in} = \text{High}$, find the power dissipation in the Driver circuit. (assume 50 Loads are connected)

Ans: $V_{in} = 12$

$\therefore T_1$ in sat.

$\therefore V_B = 0.8, V_C = 0.2$

$$\text{Now, } I_1 = \frac{12 - 0.8}{15\text{k}\Omega} = 0.747\text{mA}$$

$$I_2 = \frac{0.8 - (-12)}{100\text{k}\Omega} = 0.128\text{mA}$$

$$I_B = I_1 - I_2 = 0.619\text{mA}$$


From case (i) in ques. (a) \rightarrow

$$\therefore \text{Individual Load current} = I_L = I_{L1} = \frac{V_0 - (-12)}{(100 + 15)\text{k}\Omega} = \frac{12 - 2}{115\text{k}\Omega} = 0.106\text{mA}$$

$$\text{Total Load current} = I_S = N \times I_{L1} = 50(I_{L1}) = 5.3\text{mA}$$

In Driver circuit,
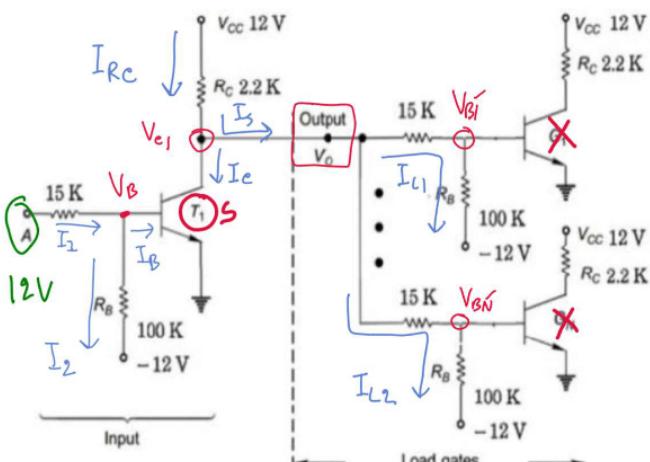
$$I_{RC} = \frac{12 - 0.2}{2.2\text{k}\Omega} = 5.3636\text{mA} \rightarrow \text{And, } I_{RC} = I_C + I_S$$



(e) If $V_{in} = \text{Low} = 0.2$, find the power dissipation in the Driver circuit.

$$V_{in} = \text{Low} = 0.2$$

T_2 in cutoff.

$\therefore V_o = \text{High}$

$\therefore G_1 \dots h_{v_{ce}} \text{ in saturation}$

Given, Fanout = 2

$$\text{From (b)} \rightarrow V_o = 9.4597V$$



In Driver, $I_B = 0$

$$I_1 = I_2 = \frac{0.2 - (-12)}{115k\Omega} = 0.106mA$$

$$I_S = \frac{12 - 9.4597}{2.2k\Omega} = 1.1547mA$$

$$\text{Power} = I_1 (I_2 + I_2) + I_S (12 - 9.4597)$$


$$= 5.477mW$$

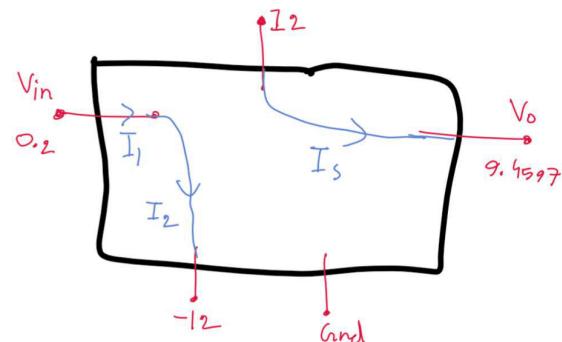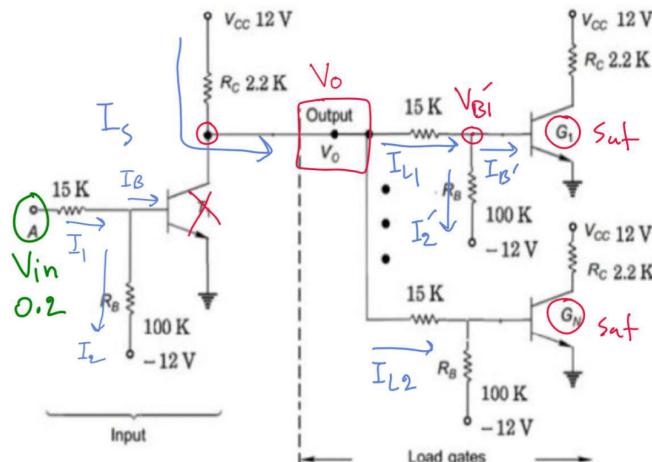

Question No. 2

For the given RTL NOR circuit assume $VOH = 1.3V$ and $VOL = 0.2V$. Also assume common emitter current gain, $\beta_F = 30$. Assume for saturation mode $VBE = 0.8V$, $VCE = 0.2V$ and cut in voltage for transistor $V_T = 0.5V$.

(a)	Find the value of maximum fanout .
(b)	Find the value of V_o (output of Driver), if Fanout(N)= 5 and Inputs A, B are Low.
(c)	Find the value of β_{min} (for Load Gates), and Power dissipation in the Driver circuit for the conditions in (b).
(d)	Find the Power dissipation in the Driver circuit when both inputs (A and B) are High.

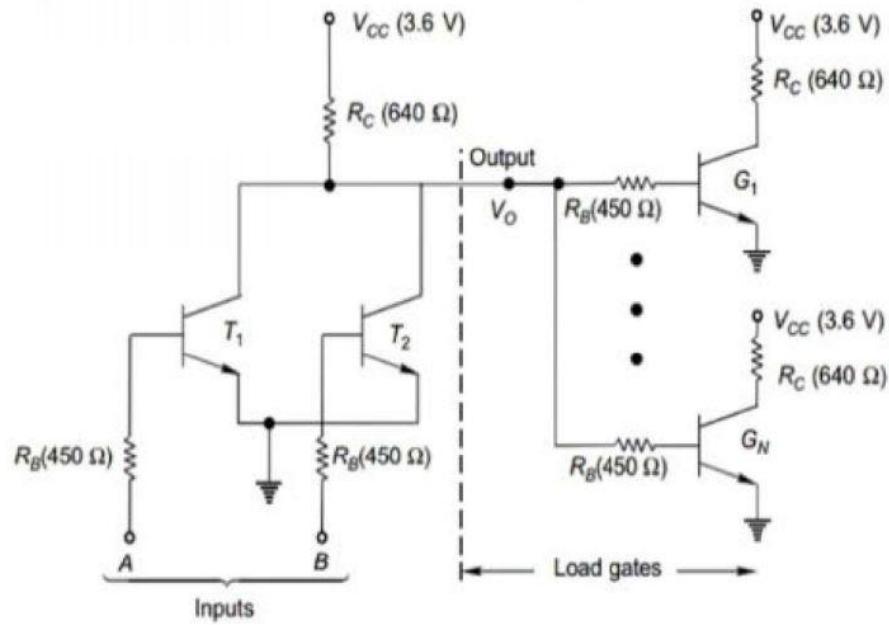

Solution:

(a) Find the value of **maximum fanout**.

Case 1: A or B or both High = 3.6V

$\therefore T_1, T_2$ in saturation

$$V_{CE} = 0.2 \rightarrow V_o = 0.2$$

\therefore Input of Load Gates = $V_o = 0.2$ = Low

$\therefore h_1, \dots, h_N$ in cutoff.

\therefore No current flow between Driver and Load.

$$\therefore \text{Fanout} = \infty.$$

Case 2: $A = B = 0.2V = \text{Low}$

T_1, T_2 OFF.

$$V_o = \text{High} = V_{OH} = 1$$

\therefore Load Gates in Saturation

$$\therefore I_{\text{Supply}} = I_3 = \frac{3.6 - V_{OH}}{640\Omega} = \frac{3.6 - 2.3}{640\Omega}$$

$$\therefore I_{\text{Supply}} = 3.593 \text{ mA}$$

$$\text{Individual Load Current, } I_L = I_{L1} = \frac{V_o - V_{B1}}{450\Omega} = \frac{1.3 - 0.8}{450\Omega} \quad [V_{BE} = 0.8 \text{ in Sat}]$$



$$\therefore I_L = 1.111 \text{ mA}$$

$$\text{Total Demand} = N(I_L)$$

$$\therefore I_{\text{Supply}} = I_{\text{Demand}} \rightarrow 3.593 = N(1.111)$$

$$\therefore N = 3.23 \rightarrow \boxed{N = 3}$$
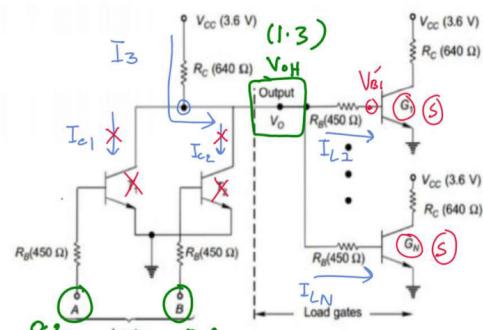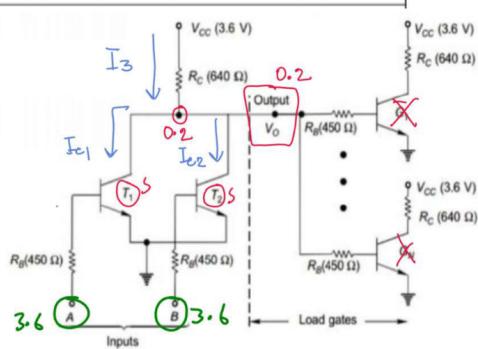
$$\therefore \text{Max Fanout} = \min(\infty, 3) = 3 \quad \boxed{\text{Ans}}$$



(b) Find the value of V_o (output of Driver), if Fanout(N)= 5 and Inputs A, B are Low.


$$A=B=0.2V = \text{Low}$$

T_1, T_2 OFF.

$V_o = \text{High}$

∴ Load Gates in Saturation
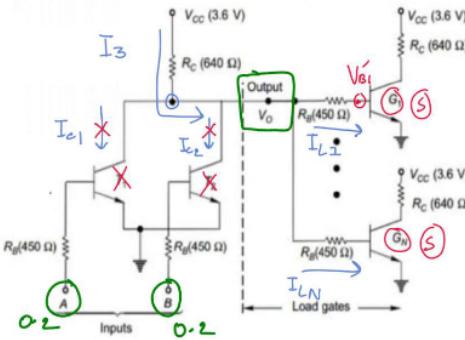
$$\therefore I_{\text{Supply}} = I_3 = \frac{3.6 - V_o}{640\Omega}$$



$$\text{Individual Load current, } I_L = I_{L2} = \frac{V_o - V_{B1}}{450\Omega} = \frac{V_o - 0.8}{450\Omega} \quad [V_{BE} = 0.8 \text{ in sat}]$$

Total Demand = $N(I_L)$

$$\therefore I_{\text{Supply}} = I_{\text{Demand}} \rightarrow \frac{3.6 - V_o}{640\Omega} = \frac{V_o - 0.8}{450\Omega} \times N$$

$$\frac{3.6 - V_o}{640} = \frac{V_o - 0.8}{450} \times 5$$

$$\therefore V_o = 1.145V \quad \boxed{\text{Ans.}}$$

(c) Find the value of β_{\min} (for Load Gates), and Power dissipation in the Driver circuit for the conditions in (b).

Soln: From (b) $\rightarrow V_o = 1.145V$

$$(i) \text{ Now, } \beta_{\min} = \frac{I_c}{I_B} \text{ (sat)}$$


Hence, Load Gates are in saturation.

For Load gate $G_1 \rightarrow$

$$V_{B1}' = 0.8 \quad \text{and,} \quad V_{c1} = 0.2$$

$$\therefore I_B = I_{L1} = \frac{V_o - V_{B1}'}{R_B} = \frac{1.145 - 0.8}{450\Omega}$$

$$\therefore I_B = 0.767mA$$

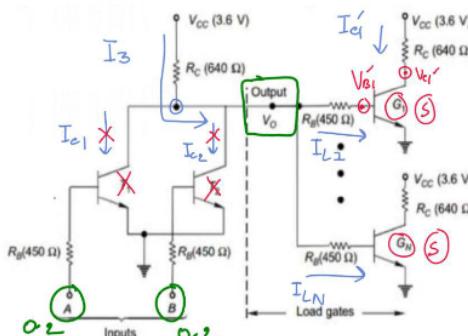


$$I_c = I_{c1}' = \frac{3.6 - V_{c1}'}{640\Omega} = \frac{3.6 - 0.2}{640\Omega}$$

$$\therefore I_c = 5.3125mA$$

$$\therefore \beta_{\min} = \frac{I_c}{I_B} = \frac{5.3125}{0.767} = 6.9263 \quad \boxed{\text{Ans.}}$$

(ii) In Driver circuit,

T_1, T_2 OFF

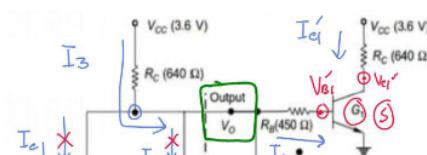

(d) Find the Power dissipation in the Driver circuit when both inputs (A and B) are High.

$$V_A = V_B = H_i = 3.6$$

$\therefore T_1, T_2$ in saturation


$$V_{BE} = 0.8 \rightarrow V_B = V_{B2} = 0.8$$

$$V_{CE} = 0.2 \rightarrow V_{C1} = V_{C2} = V_o = 0.2$$

∴ Input of Load Cycles = $V_0 = 0.9 = 1.25$

∴ h_1, \dots, h_N in cutoff.

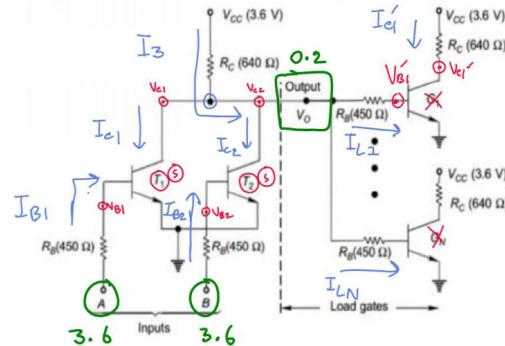∴ No current flow between Driver and Load





$$\text{Now, } I_{B1} = \frac{3.6 - V_{B1}}{450\Omega} = \frac{3.6 - 0.8}{450\Omega} = 6.222 \text{ mA}$$

$$I_{B2} = \frac{3.6 - V_{B2}}{450\Omega} = \frac{3.6 - 0.8}{450\Omega} = 6.222 \text{ mA}$$

$$I_3 = \frac{3.6 - 0.2}{640} = 5.312 \text{ mA}$$
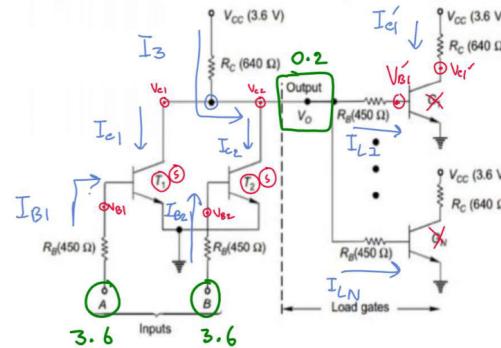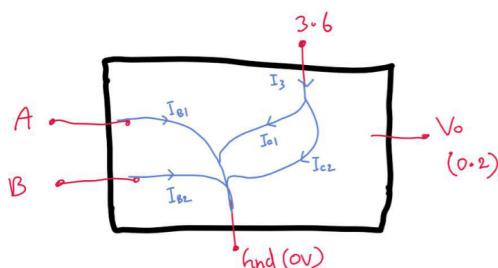
$$I_{c1} = I_{c2} = \frac{I_3}{2} = 2.656 \text{ mA}$$




$$\begin{aligned}
 \text{Power} &= \sum \Delta V I = I_{B1}(V_{B1-0}) + I_{B2}(V_{B2-0}) + \underbrace{I_{C1}(3.6-0) + I_{C2}(3.6-0)}_{= I_3(3.6-0)} \\
 &= I_{B1}(V_{B1-0}) + I_{B2}(V_{B2-0}) + I_3(3.6-0) \\
 &= 63.922 \text{ mW}
 \end{aligned}$$

Question No. 3

For the given RTL inverter circuit assume $V_{OH}=11.5\text{ V}$ and $V_{OL}=0.2\text{ V}$. Also assume common emitter current gain, $\beta_F=30$. Assume for saturation mode $V_{BE}=0.8\text{ V}$, $V_{CE}=0.2\text{ V}$ and cut in voltage for transistor $V_{\gamma_T}=0.5\text{ V}$.

(a)	Find the value of V_{IL} in V .
(b)	Find the value of V_{IH} in V .
(c)	Find the value of Noise margin, V_N in V .

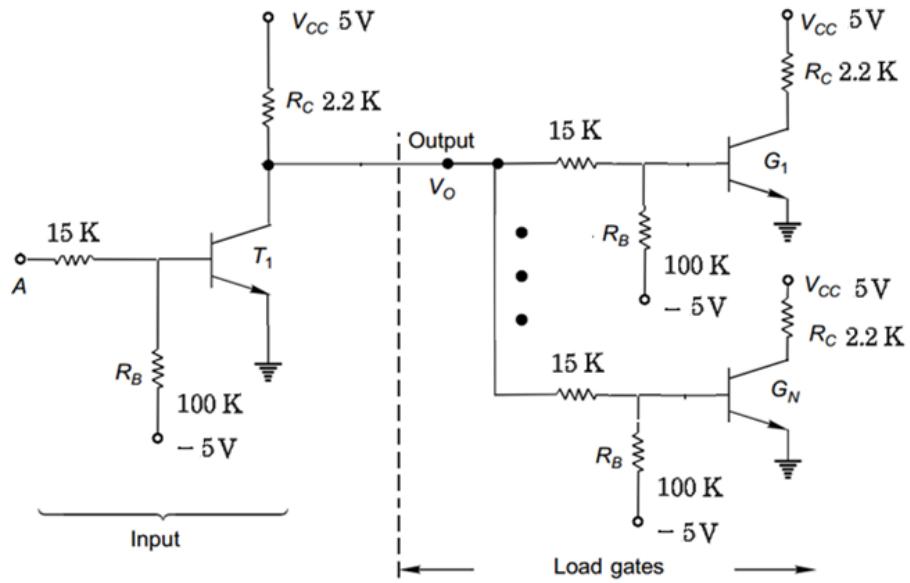


Solution:


Soln: We can ignore Load gates for noise margin calculation.

$V_{IL} \rightarrow T_1$ in cutoff

$\therefore I_{Rc} = I_c$.

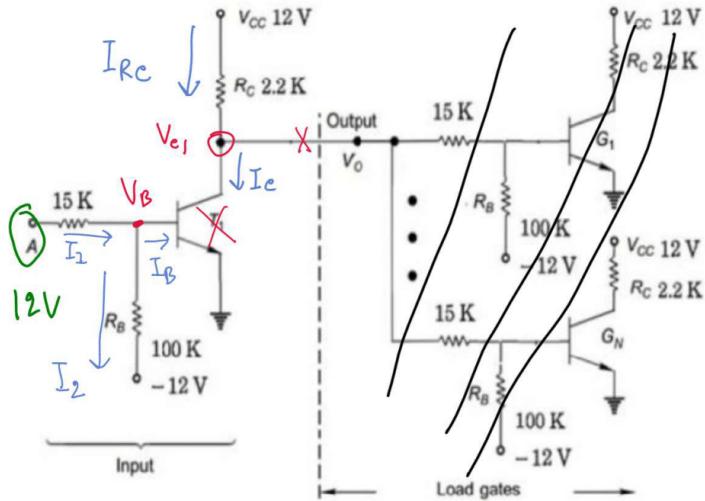

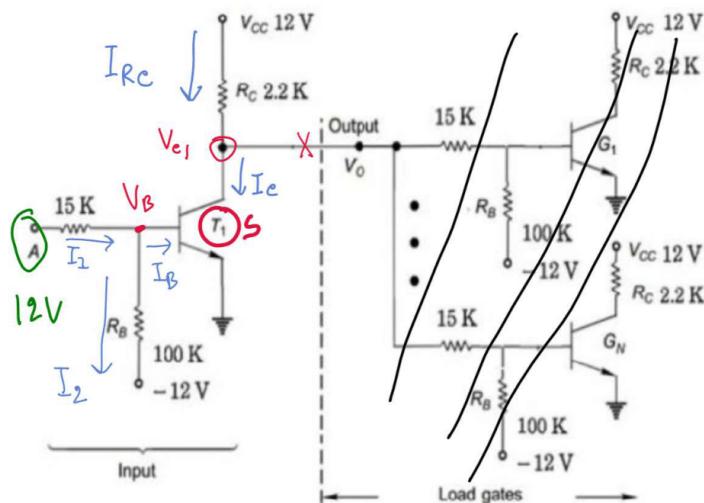$V_{IH} \rightarrow T_1$ in between Active and Saturation (edge of saturation)



$$V_{OL} = 0.2 \rightarrow V_{CEsat}$$

V_{OH} → depends on design requirements

Will be given in question

Here, we will use $V_{OH} = \frac{12 - 0.5}{12 - 0.5} \times 12 = 11.5V$

$$V_{OH} = 11.5V$$

④ V_{IL} calculation → $V_{IL} = 0.5V$

BJT just turns on for cut-in volt

$$V_{BE} = 0.5V$$

$$\therefore V_B = 0.5V$$

at this point, $I_B = 0A$

$$\therefore I_1 = I_2 \quad I_2 = \frac{0.5 - (-12)}{100k} = 0.125mA$$

$$I_1 = \frac{V_i - 0.5}{15k} = I_2 = 0.125mA$$

$$\hookrightarrow V_i = 2.375 = V_{IL} \text{ (max)}$$

* V_{IH} calculation:

BJT going from saturation \xrightarrow{I} active

edge V_{IH} of saturation

\therefore Both formulas for sat and active mode can be applied.

$$V_B = 0.8$$

$$V_C = 0.2 \quad I_C = \beta I_B$$

30 Ω

$$I_C = \frac{12 - 0.2}{2.2k} = 5.3636 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{5.3636}{30} = 0.1788 \text{ mA}$$

$$I_2 = \frac{0.8 - (-12)}{100k} = 0.128 \text{ mA}$$

$$I_1 = I_2 + I_B = (0.128 + 0.1788)$$

$$= 0.3068 \text{ mA}$$

$$I_{D_s} = \frac{V - 0.8}{15k} = 0.3068 \text{ mA}$$

$$\therefore V = 5.4081 \text{ V} = V_{I_H}$$

$$\therefore V_{NH} = V_{O_H} - V_{I_H} = 12.5 - 5.4081 = 6.0982 \text{ V}$$

$$V_{NL} = \frac{V_{IL} - V_{OL}}{2.375 - 0.210} = \frac{12.0 - 0.210}{2.375 - 0.210} = 2.175 \text{ V}$$


$$\text{Noise Margin} = \text{Minimum} \rightarrow V_h = 2.175 \text{ V}$$

$$= \text{Min}(6.098, 2.175) = 2.175 \text{ V}$$

Question No. 4


AND Gate: If $V(0) = 0V$ and $V(1) = 5V$,
ans $R_s = 0.25 k\Omega$, $R = 100 k\Omega$. Fan In N = 2

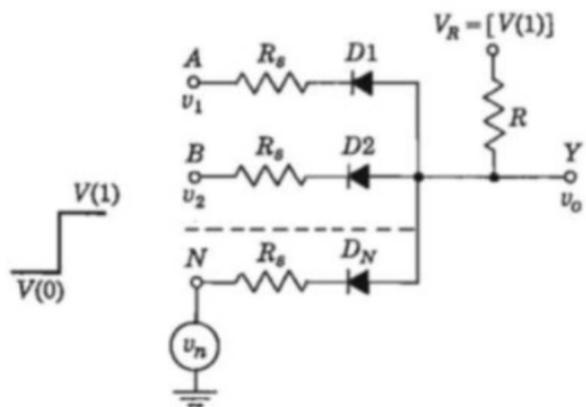- (a) Find out the output voltage levels.
(b) Find out the maximum power dissipation.



Solution:

Activate Window

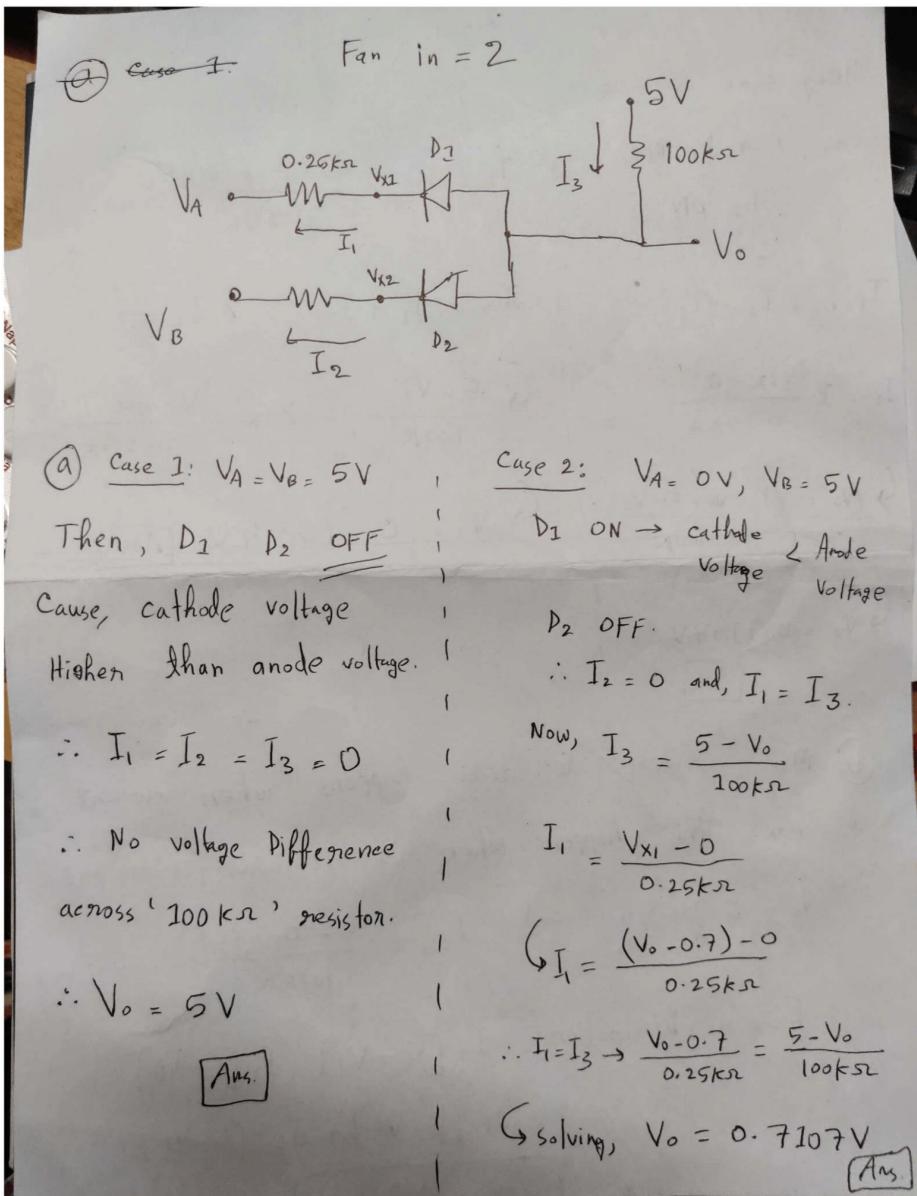

Case 3: $V_B = 0, V_A = 5V$

Case 4: $V_A = 0, V_B = 0$

Using same logic as

case 2 $\rightarrow D_1$ OFF

D_2 ON

D_1 D_2 ON

$$I_1 = I_2 = \frac{V_o - 0.7}{0.25k}$$

$$I_1 = 0, I_2 = I_3$$

$$I_3 = I_1 + I_2 = 2I_1$$

$$I_2 = \frac{V_{x2} - 0}{0.25k\Omega}$$

$$\frac{5 - V_o}{100k} = 2 \times \frac{V_o - 0.7}{0.25k}$$

$$\frac{(V_o - 0.7)}{0.25k} = \frac{5 - V_o}{100k}$$

$$\rightarrow V_o = 0.7054V$$

$$\rightarrow V_o = 0.7107V$$

Ans.

(b) Max power dissipation happens when current is max. This happens when V_o is lowest (Case 04).

$$\therefore V_o = 0.7054V \text{ and, } I_3 = \frac{5 - 0.7054}{100k\Omega} = 0.0429mA$$

$$\therefore \text{Power Dissipation} = I_3 [5 - V_A] = I_3 [5 - V_B]$$

$$= I_1 [5 - V_A] + I_2 [5 - V_B]$$

$$= 0.2147 \text{ mW}$$

